

Phase Margin

Pedavegi Aditya*

Consider an op amp having a single pole open loop response $G_0 = 10^5$ and $f_p = 10$ Hz. Let the OPAMP be ideal connected in non-inverting terminal with a nominal low frequency of closed loop gain of 100

- 1) A manufacturing error introducing a second pole at 10 kHz. Find the frequency at which $|GH| = 1$ and the corresponding phase margin.
- 2) For what values of H is the phase margin greater than 45° ?

1. Find the transfer function of the two pole OPAMP.

Solution: For a two-pole amplifier open loop transfer function is

$$G(s) = \frac{G_0}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)} \quad (1.1)$$

Poles are at $f_1 = 10$ and $f_2 = 10^4$

$$G(f) = \frac{G_0}{\left(1 + j\frac{f}{f_1}\right)\left(1 + j\frac{f}{f_2}\right)} \quad (1.2)$$

$$= \frac{10^5}{\left(1 + j\frac{f}{10}\right)\left(1 + j\frac{f}{10^4}\right)} \quad (1.3)$$

2. Find the feedback H .

Solution: Since the closed loop gain

$$|T| = 100 \quad (2.1)$$

and for nominal low frequency $|GH| \gg 1$,

$$H \approx \frac{1}{|T|} = 0.01 \quad (2.2)$$

3. Find the PM and the crossover frequency.

Solution: From (1.3) and (2.2)

$$|GH| = 1 \quad (3.1)$$

$$\Rightarrow \frac{10^3}{\left(\sqrt{1 + \frac{f^2}{100}}\right)\left(\sqrt{1 + \frac{f^2}{10^8}}\right)} = 1 \quad (3.2)$$

$$\text{or } f_{180} = 7.8615 \text{ kHz.} \quad (3.3)$$

using the following python code.

```
codes/ee18btech11034/ee18btech11034.py
```

From (1.3), $\therefore \angle H = 0^\circ$,

$$\angle G(f)H(f) = \angle G(f) \quad (3.4)$$

$$- \tan^{-1}\left(\frac{f}{10}\right) - \tan^{-1}\left(\frac{f}{10^4}\right) \quad (3.5)$$

$$\Rightarrow PM = 180^\circ + \angle G(f_{180}) \quad (3.6)$$

$$= 180^\circ - 128.1^\circ = 51.9^\circ \quad (3.7)$$

4. Verify your result using a Bode plot.

Solution: The following code generates Fig. 4

```
codes/ee18btech11034/ee18btech11034_1.py
```

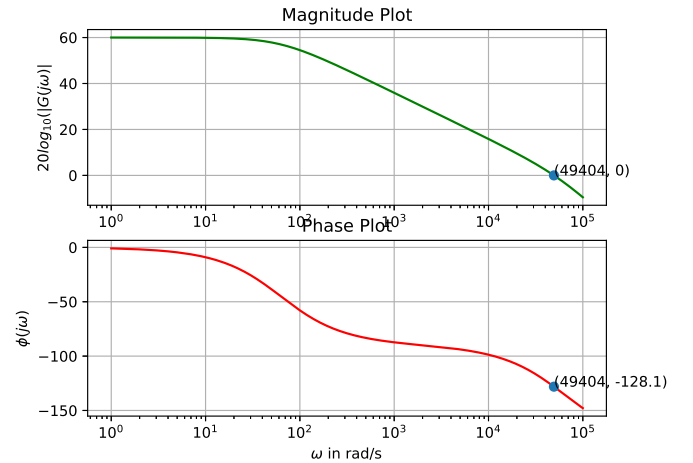


Fig. 4

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

5. Realise the above system with $PM = 51.9^\circ$ using a feedback circuit.

Solution:

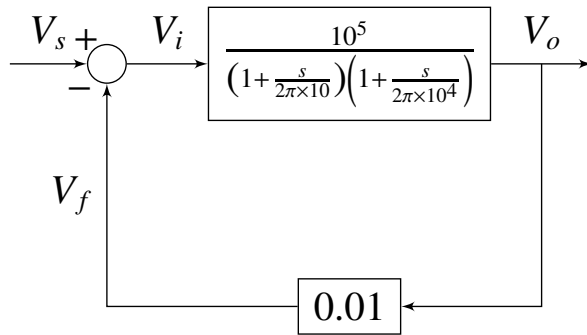


Fig. 5

The transfer function of OPAMP is

$$G(s) = \frac{10^5}{\left(1 + \frac{s}{2\pi \times 10}\right)\left(1 + \frac{s}{2\pi \times 10^4}\right)} \quad (5.1)$$

6. For the feedback gain H

Solution:

Choose a resistance network such that

$$H = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2} \approx 0.01 \quad (6.1)$$

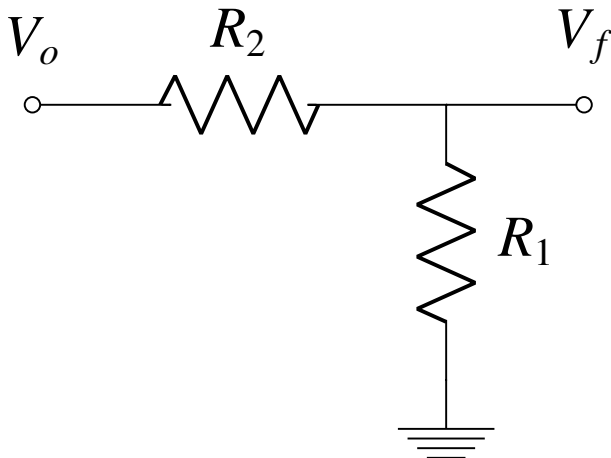


Fig. 6

Choose R_1 and R_2 as

$$R_1 = 10\Omega \quad (6.2)$$

$$R_2 = 990\Omega \quad (6.3)$$

$$H = \frac{R_1}{R_1 + R_2} = \frac{10}{10 + 990} = 0.01 \quad (6.4)$$

7. Feedback Circuit for $PM = 51.9^\circ$

Solution:

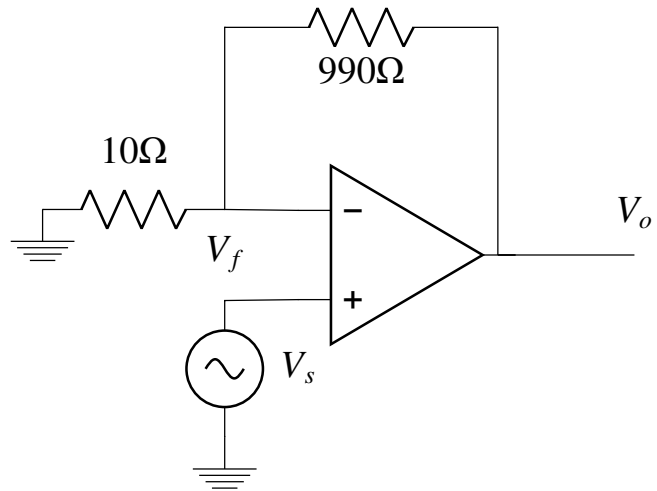


Fig. 7

8. Find H such that $PM = 45^\circ$.

Solution: From (3.4), assuming constant H ,

$$\angle G(f_{180}) = 45^\circ - 180^\circ = -135^\circ \quad (8.1)$$

$$\Rightarrow -\tan^{-1}\left(\frac{f}{10}\right) - \tan^{-1}\left(\frac{f}{10^4}\right) = -135^\circ \quad (8.2)$$

$$\Rightarrow \frac{\frac{f}{10} + \frac{f}{10^4}}{1 - \frac{f^2}{10^5}} = -1 \quad (8.3)$$

$$\text{or, } f_{180} \approx 10 \text{ kHz} \quad (8.4)$$

From (1.3),

$$\because |G(f_{180})H| = 1, \quad (8.5)$$

$$\frac{(10^5)H}{\left(\sqrt{1 + \frac{10^8}{100}}\right)\left(\sqrt{1 + \frac{10^8}{10^8}}\right)} = 1 \quad (8.6)$$

$$\Rightarrow H = 1.414 \times 10^{-2} \quad (8.7)$$

$$\text{or, } H_{\max} = 1.414 \times 10^{-2} \quad (8.8)$$

which is the value of H for which $PM > 45^\circ$.

9. Verify the above using a Bode plot.

Solution: The following code plots Fig. 9.

codes/ee18btech11034/ee18btech11034_2.py

The transfer function of OPAMP will be unchanged. For the required feedback gain H the feedback circuit changes

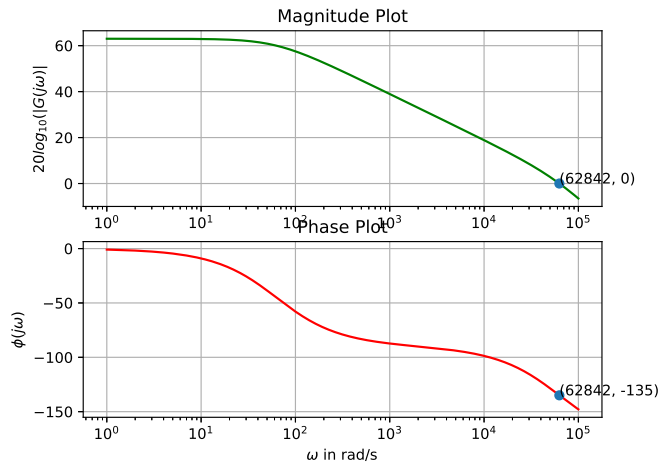


Fig. 9

10. Realise the above system with $PM = 45^\circ$ using a feedback circuit.

Solution:

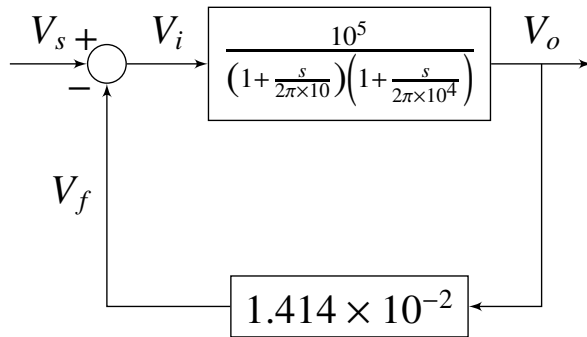


Fig. 10

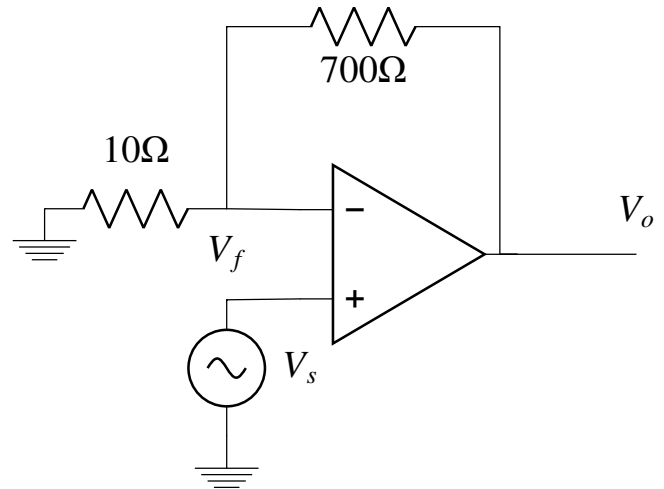


Fig. 12

11. For the feedback gain H

Solution:

$$R_1 = 10\Omega \quad (11.1)$$

$$R_2 = 700\Omega \quad (11.2)$$

$$H = \frac{R_1}{R_1 + R_2} \Rightarrow \frac{10}{10 + 700} \approx 1.41 \times 10^{-2} \quad (11.3)$$

12. Feedback Circuit for $PM = 45^\circ$

Solution: